
Full Custom IC Design


Cadence Virtuoso

Ph. D. ByoungJin Lee

 

4*1 MUX (MUltipleXer)


VLSI Circuits Design Example

 

CONTENTS

Tools

 Cadence Virtuoso Schematic Editor / Layout Editor
Cadence Virtuoso Spectre / ADE
Assura DRC / LVS
GPDK090



순 서

- 4*1 MUX
- Circuit design(logic gate, Switch)
- Schematic
- Circuit simulation
- Layout
- DRC, LVS

4*1MUX(Multiplexer)


• 복수회로에서 입력되는 4개의 신호 중 어느 하나의 입력신호를 선택하여 출력회로에 내보내주는 논리 회로

OUT =
$$\overline{S1}\overline{S0}A + \overline{S1}S0B + S1\overline{S0}C + S1S0D$$


MUX 진리표			
S1	S0	OUT	
0	0	A	
0	1	В	
1	0	С	
1	1	D	

구현 방법

 
- CMOS Tr.로 스위치를 구현하여 4*1 MUX를 구성하였다.
- Tr.의 수를 줄일 수 있는 장점이 있다.
 - Logic gate
 - (Inverter) (2*2) + (3Nand) 4*6 + (4Nand) 1*8 = 36개
 - CMOS switch
 - (CMOS) 2*6 + (Inverter) 2*2 = 16개




Schematic(Logic gate)

 


Schematic(Switch)

 


4*1 MUX simulation setup

 


Wave Form

 


Wave Form

 


4*1 MUX 블록 외부 PORT

 


Inverter Schematic

 


Switch Schematic

 

Inverter (Layout)

 


Inverter (DRC)

 





Inverter (LVS)

 

Switch (Layout)

 


Switch (DRC)

 





Switch (LVS)

 


4*1 MUX Layout(logic gate)

 

4*1 MUX Layout

 


4*1 MUX DRC(logic gate)

 





4*1 MUX LVS(logic gate)

 


4*1 MUX Layout(Switch)

 

4*1 MUX Layout(Switch)

 


4*1 MUX DRC(Switch)

 



4*1 MUX LVS(Switch)

 

크기비교

	Logic gate	Switch
가로(um)	13.38	6.37
세로(um)	7.4	7.56

	Logic gate	Switch
Tr. 수	36	16
Tr. 수		20개 감소

